

45V to 345V Boost Converter Example using GPI65015TO LTSPICE Model




GANPOWER INTERNATIONAL


Schematic

Boost Converter:

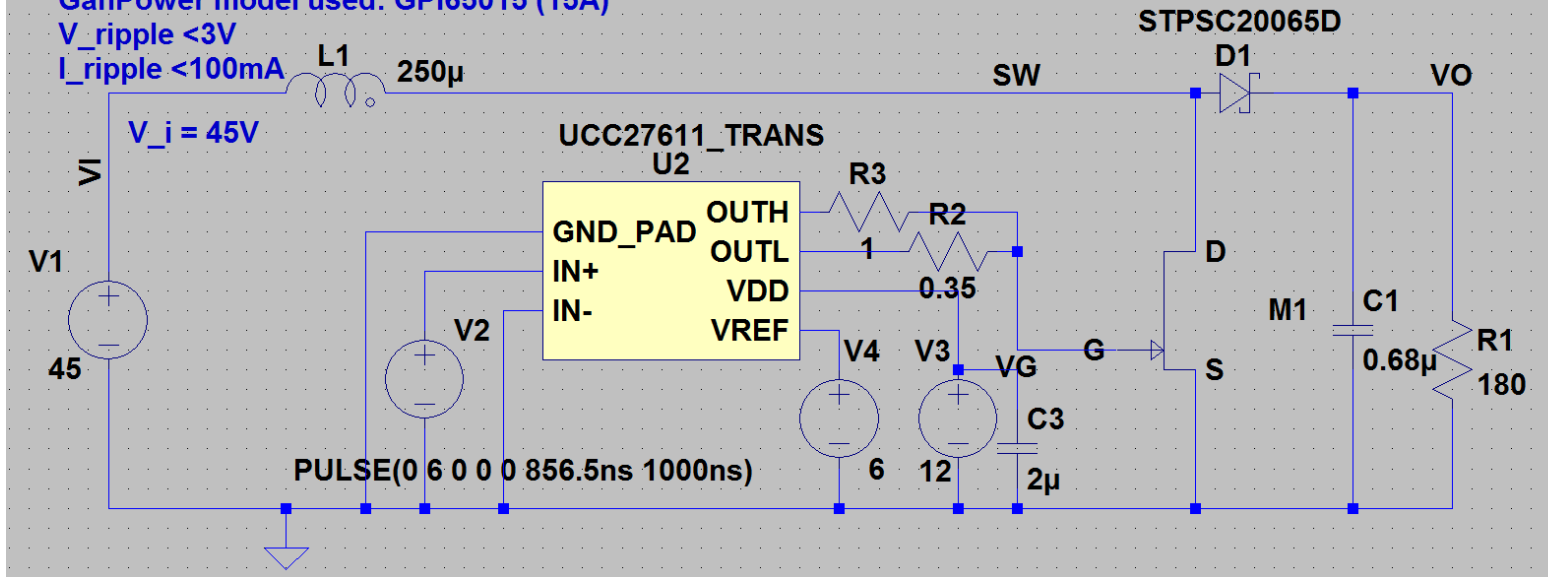
$V_{in} = 45\text{ V}$
 $V_{out} = 345\text{ V}$
 $I_{in} = 16.4\text{ A}$
 Gate driver = UCC27611
 GanPower model used: GPI65015 (15A)
 $V_{ripple} < 3\text{ V}$
 $I_{ripple} < 100\text{ mA}$



Output Voltage and Current

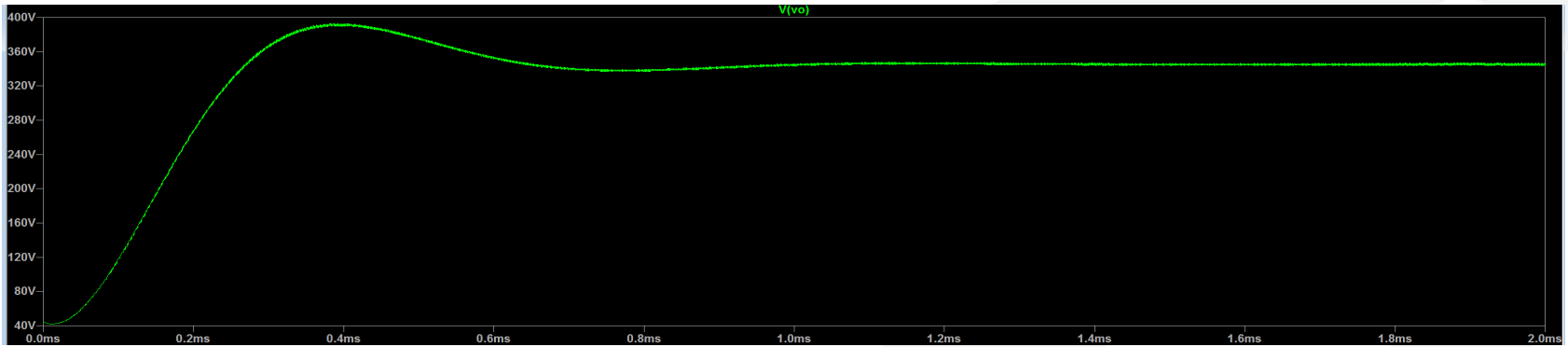


V_{out} Plot (V)

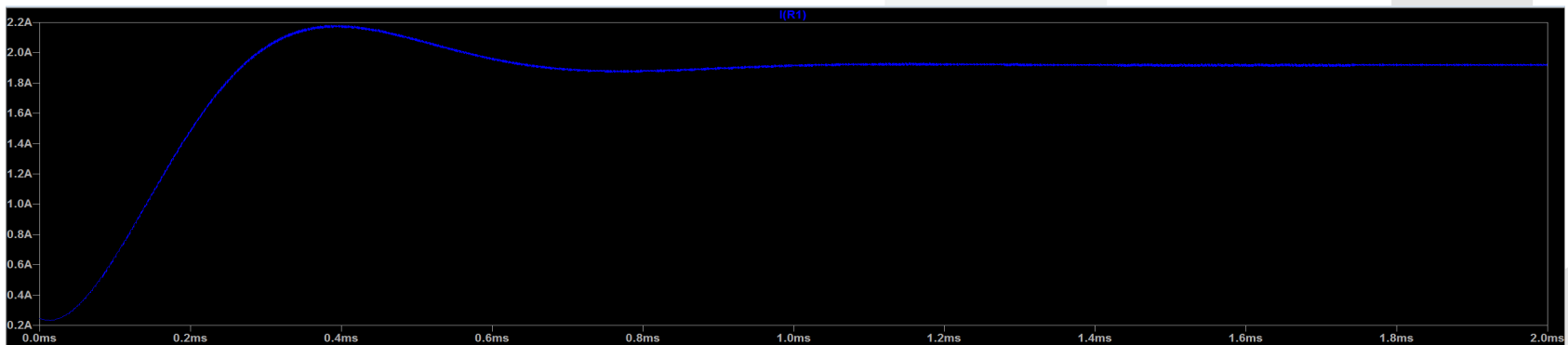

I_{out} Plot (V)

Input Voltage and Current

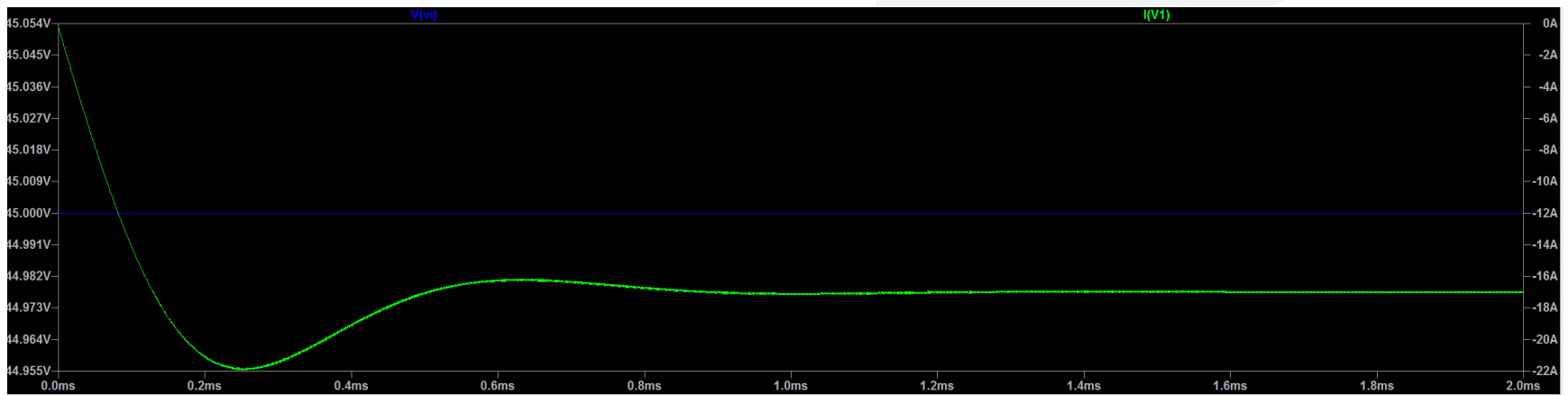

V_{in} Plot (V) Blue
 I_{in} Plot (A) Green

Duty Cycle and Frequency

- $\frac{V_{out}}{V_{in}} = \frac{1}{1-D} = \frac{345V}{45V} \rightarrow D = 0.87$


- Frequency (1MHz)

- Theoretical: $T_{on} = 870ns$, $T_{period} = 1000ns$

- Simulated: $T_{on} = 856.5ns$, $T_{period} = 1000ns$


Gate Driver Requirements

- UCC27611 is a high speed gate driver for E-mode GaN devices
- 2uF ceramic bypass capacitor should be connected between VDD and GND per the data sheet
- OUTH and OUTL are connected in parallel to the gate of the transistor
- IN+ supplies a positive voltage signal to the driver
- GND_PAD is referenced to the ground node
- The transistor is driven with a 6V pulse
- VDD requires a 12V power supply
- Set R_OH to 1 Ohm and ROL to 0.35 Ohms

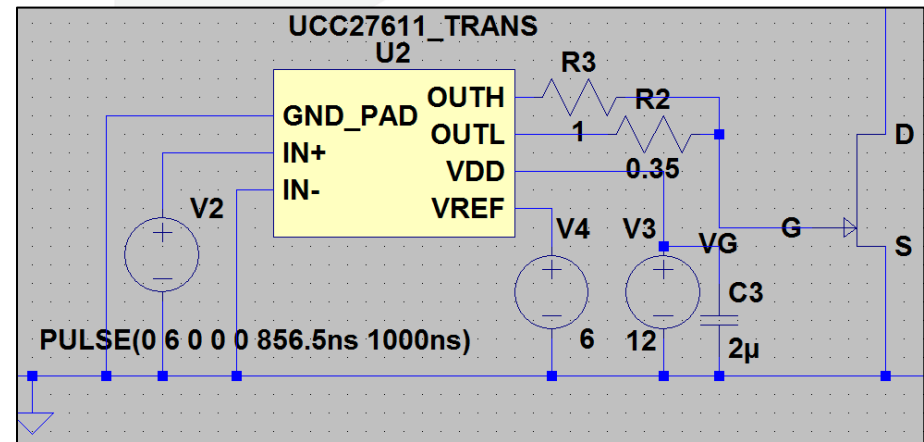

Diode (STPSC20065)

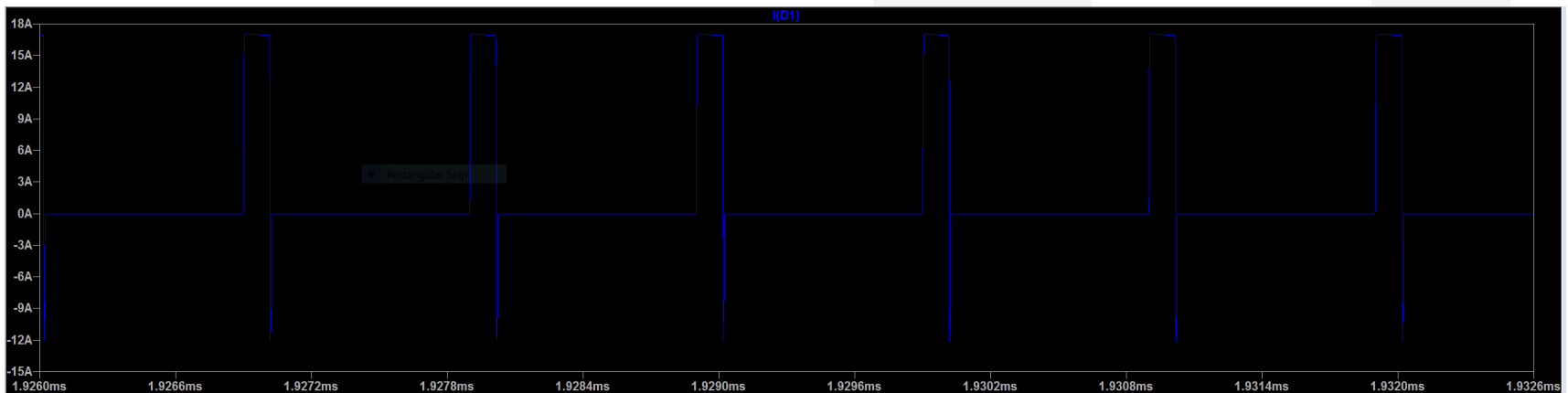
- SiC Diode with high breakdown voltage (650V) and max current (20A)
- Schottky Diode for fast switching times and minimal power loss (~ns)
 - ~2.5W power loss at steady state compared to ~700W output
 - 1.6V forward voltage drop



Diode Current Plot (A) **Blue**

Inductance and Inductor Ripple

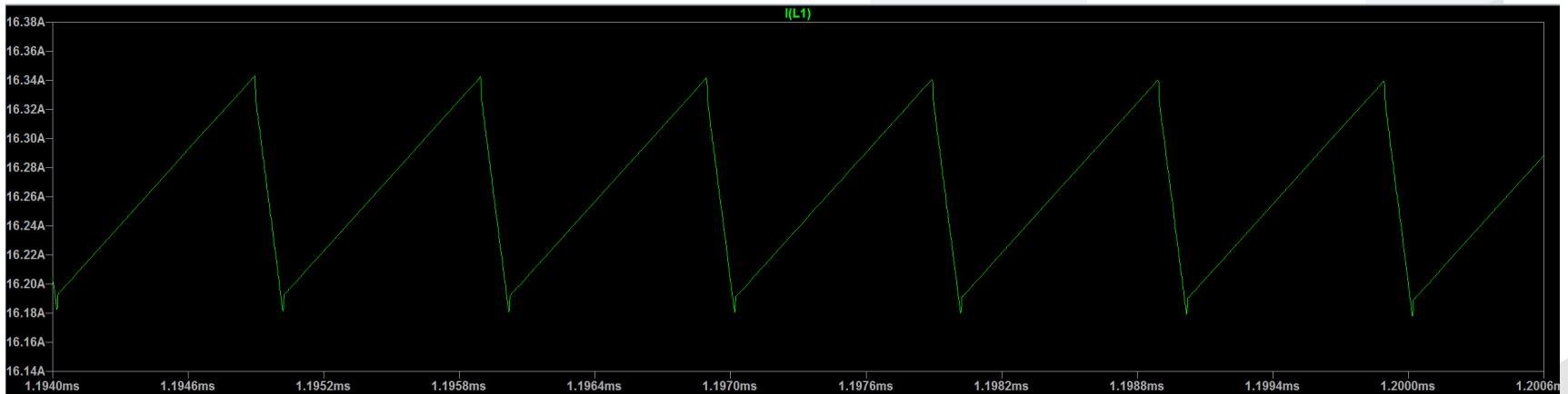
- Inductor Ripple less than 100mA
- $L = \frac{(V_{in} - V_{out}) * D}{f_s * \Delta I_L}$ Choose L = 250uH
- Current rating > 20A (Abracon ATCA-08-251M-H), ESR = 27 mOhms
- Favour inductors with lower ESR (more power efficient)



Inductor Current Plot (A) Green

Capacitor and Voltage Ripple

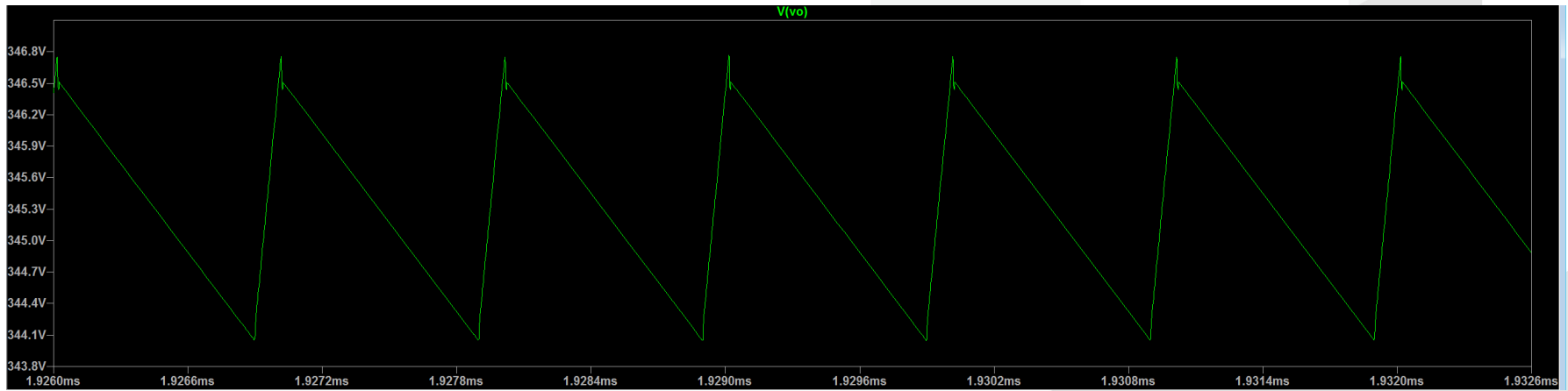
- Voltage ripple less than 3V (C = 0.58uF)
- $C = \frac{I * D}{f_s * \Delta V_{out}} = 0.58\mu F$ (Adjusted to 0.68uF after simulation)
- Voltage rating > 350V and current rating > 5A RMS
- Lower series resistance reduces output voltage ripple
 - Chose capacitor with 10 mOhm ESR and 450V rating
 - (Murata KR355TD72W684MH01)



Capacitor Voltage Plot (V) Green

Power Efficiency

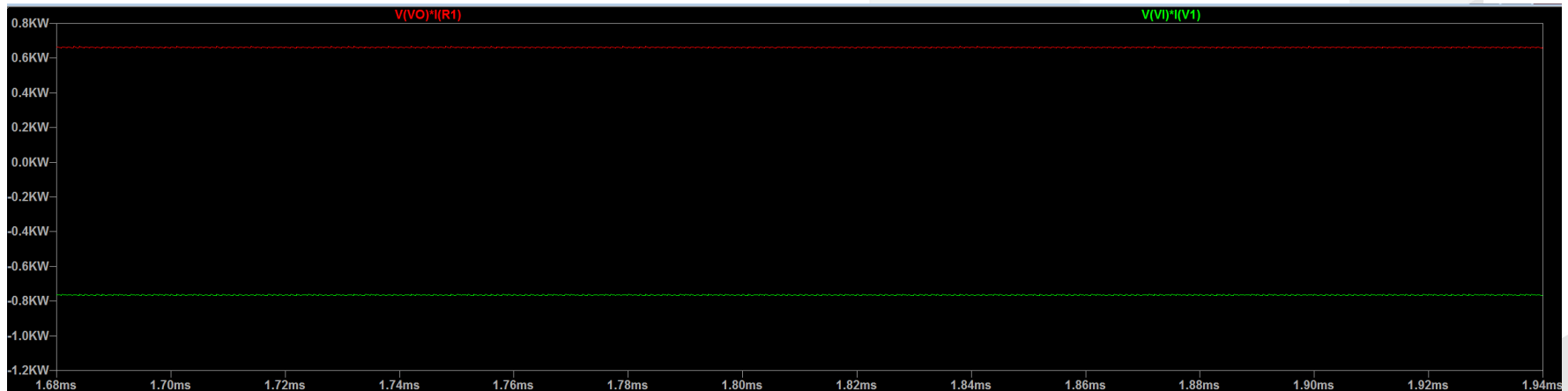- $eff = P_{out}/P_{in} = 660W/730W = 90\%$ (steady state)
- Largest power losses are due to the inductor and transistor
 - Inductor (8W) and Transistor (60W)
 - Capacitor (75mW) and Diode (2.5W)



Input Power **Green**
 Output Power **Red**