

Simulation of a full-bridge inverter using 1200V GaNFET


- Effect of dead time and load inductance



Applicable GaNPower GaNFET:
GPIHV15DK;
GPIHV30DDP5L

GANPOWER INTERNATIONAL
鎳能國際半導體有限公司

Dec. 2019

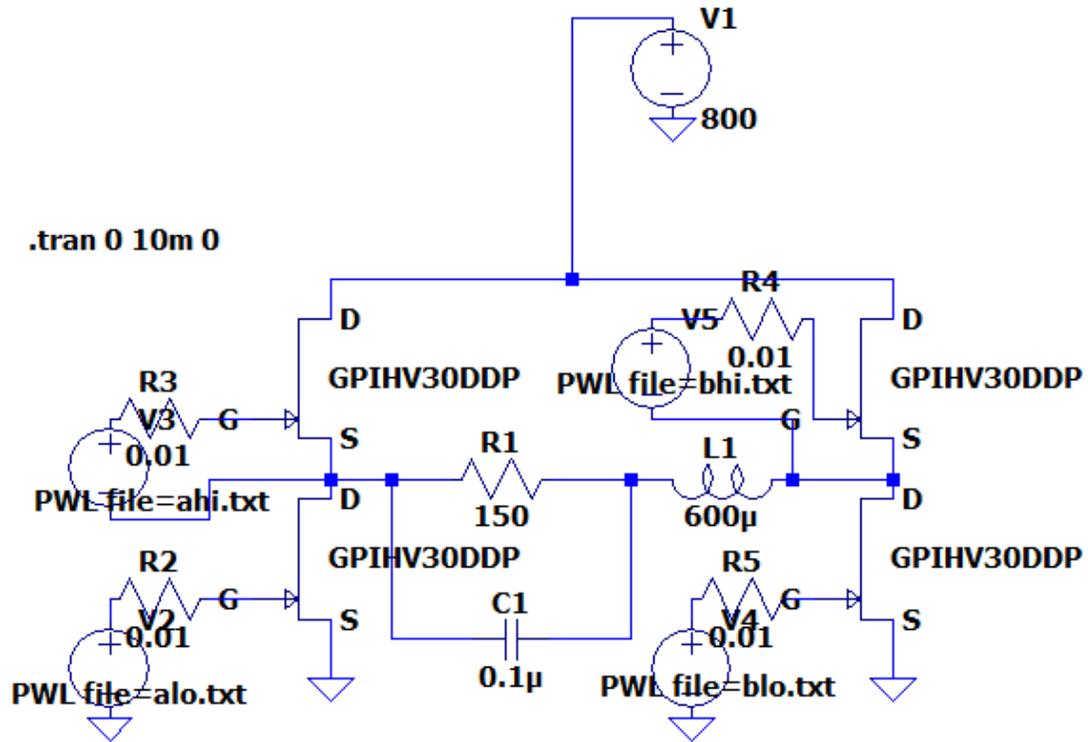

C:\deadtme40ns\full>sine_modulation.exe

==>GaNPower sine wave modulation program<==

For tech support: iganpower.com

This program uses input_fullbr.txt as input

Explanation is contained within the input file.



The output is PWM waveform for two half-bridge a,b

Output files: alo.txt, ahi.txt

Output files: blo.txt, bhi.txt

==> Please enter to generate data

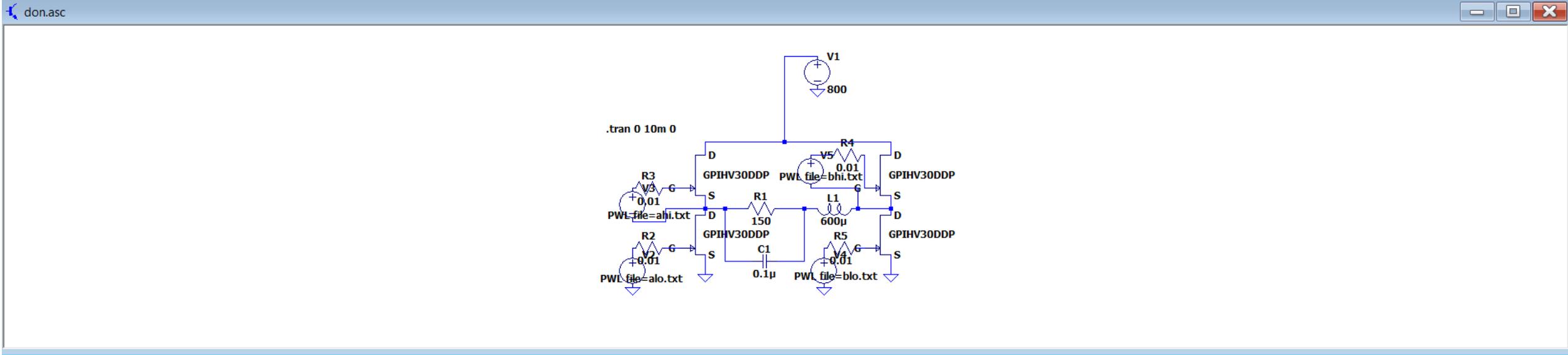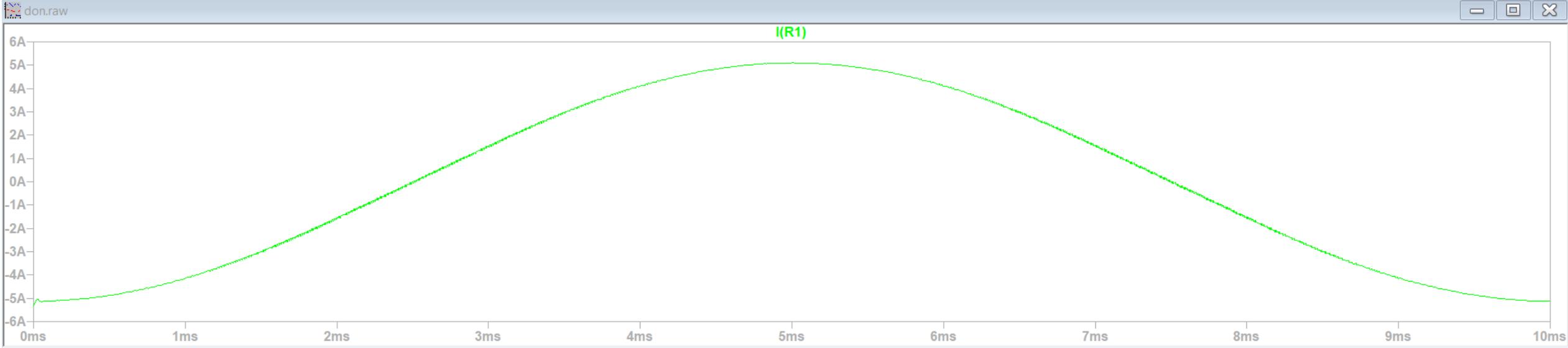- 6. #vmax --- full-bridge inverter PWM generator input
- 40.e-9 #deadtime or leadtime
- 5.e-9 #rise/fall time
- 100. #ACline frequency for one halfbridge
- 90. #ACline sine wave initial phase angle in degrees
- 250000. #switching freq
- 3 #number of ACline cycle to generate PWM
- 9999 #if positive, the on-time of double pulse trigger pulse



```
C:\deadtime40ns\full>halfbridge_power_Itspice.exe
```

```
Welcome to GaNPower Half Bridge
```

```
Power Loss Calculator
```

```
Input control is input.txt
```

```
Please hit return to run the calculator or  
enter i for information on the calculator
```

```
-->> Average  $V_d \cdot I_d$  power loss:
```

```
Power loss for low side (W)= 5.01576953227360
```

```
Power loss for hi side (W)= 4.91863864512995
```



```
Average load power (W)= 1926.83165786620
```

```
Percent power loss= 0.515582569802961
```



 X2 for full-bridge

```
-->>
```

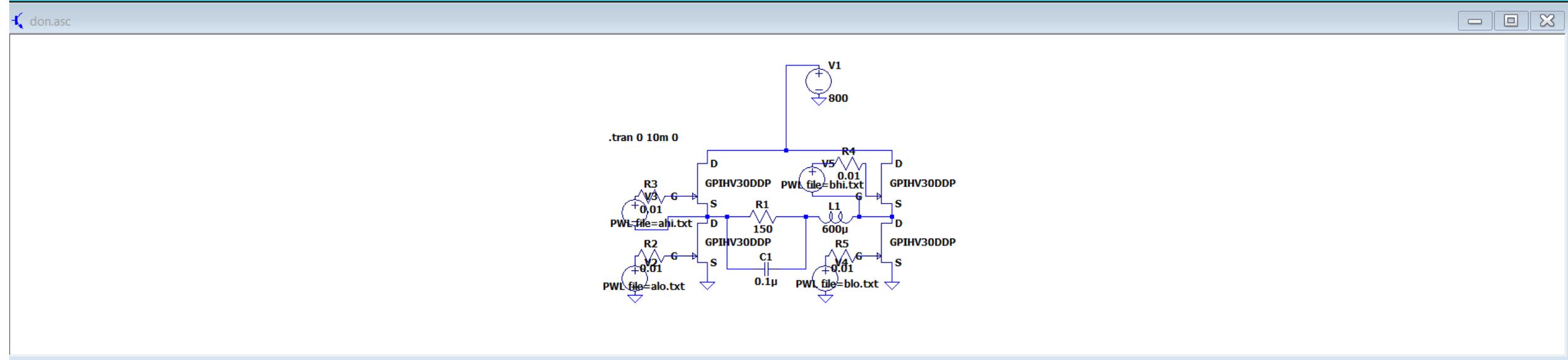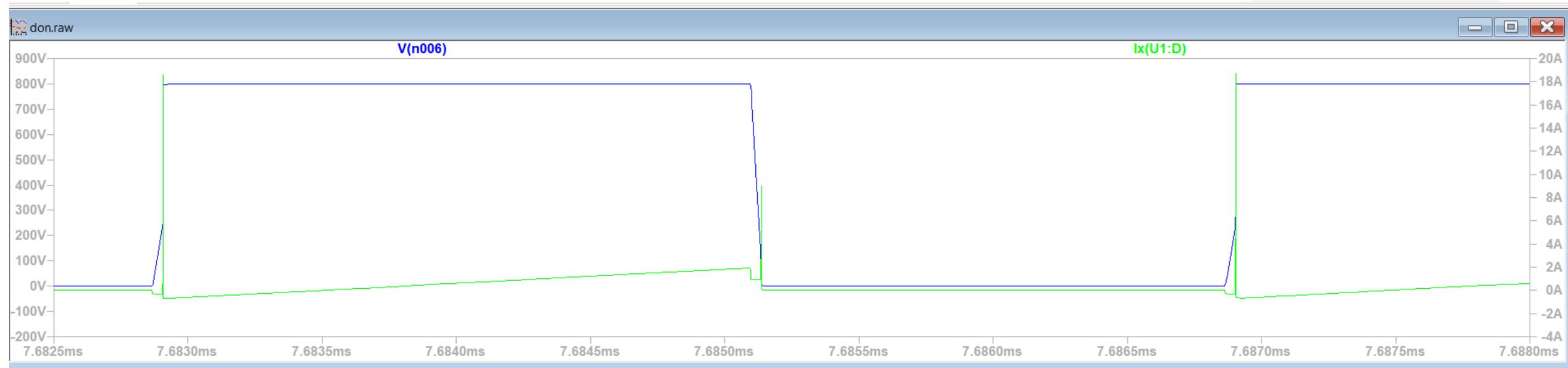
```
Please enter again to close the program
```



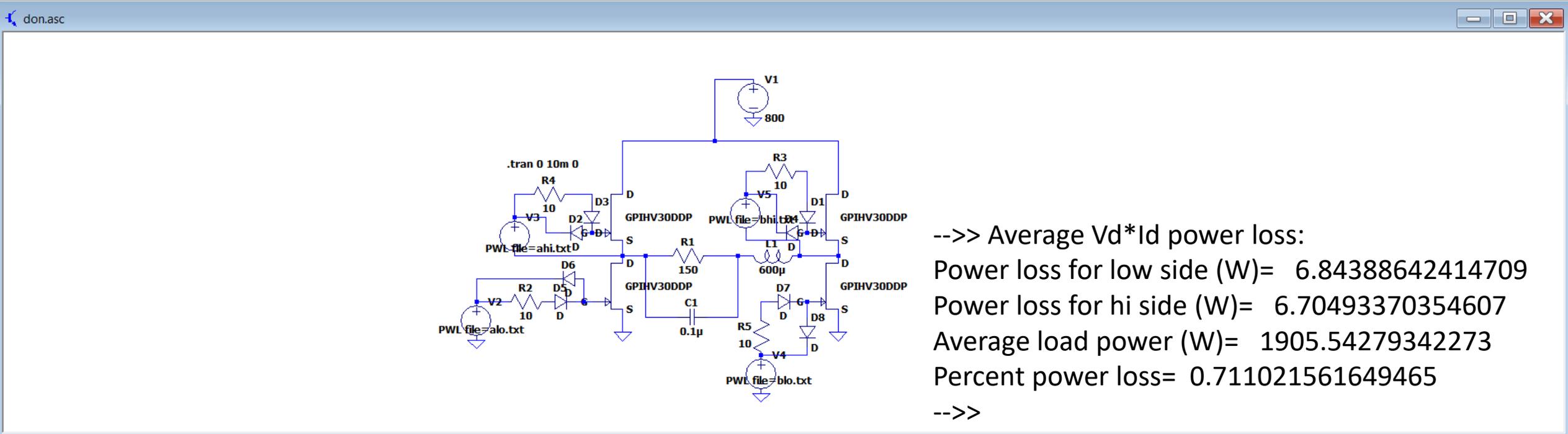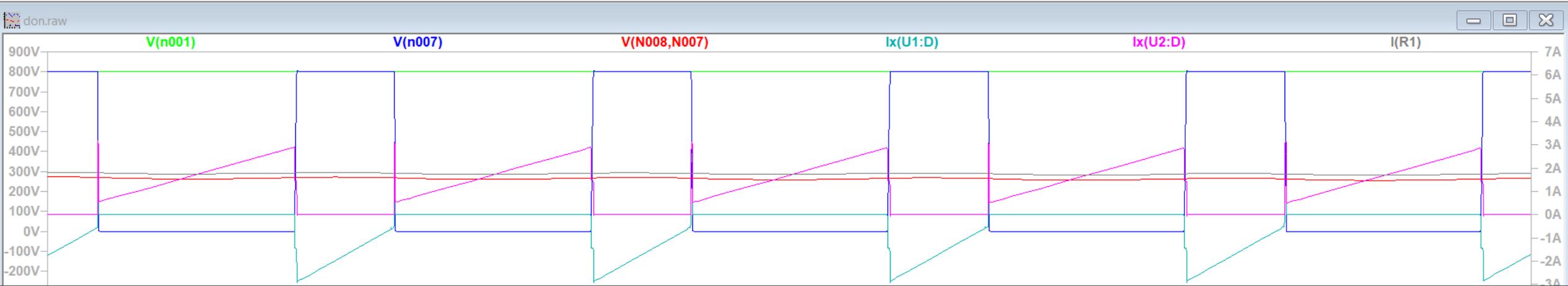Charging gate resistors do not help improve power efficiency for GaNFET switch




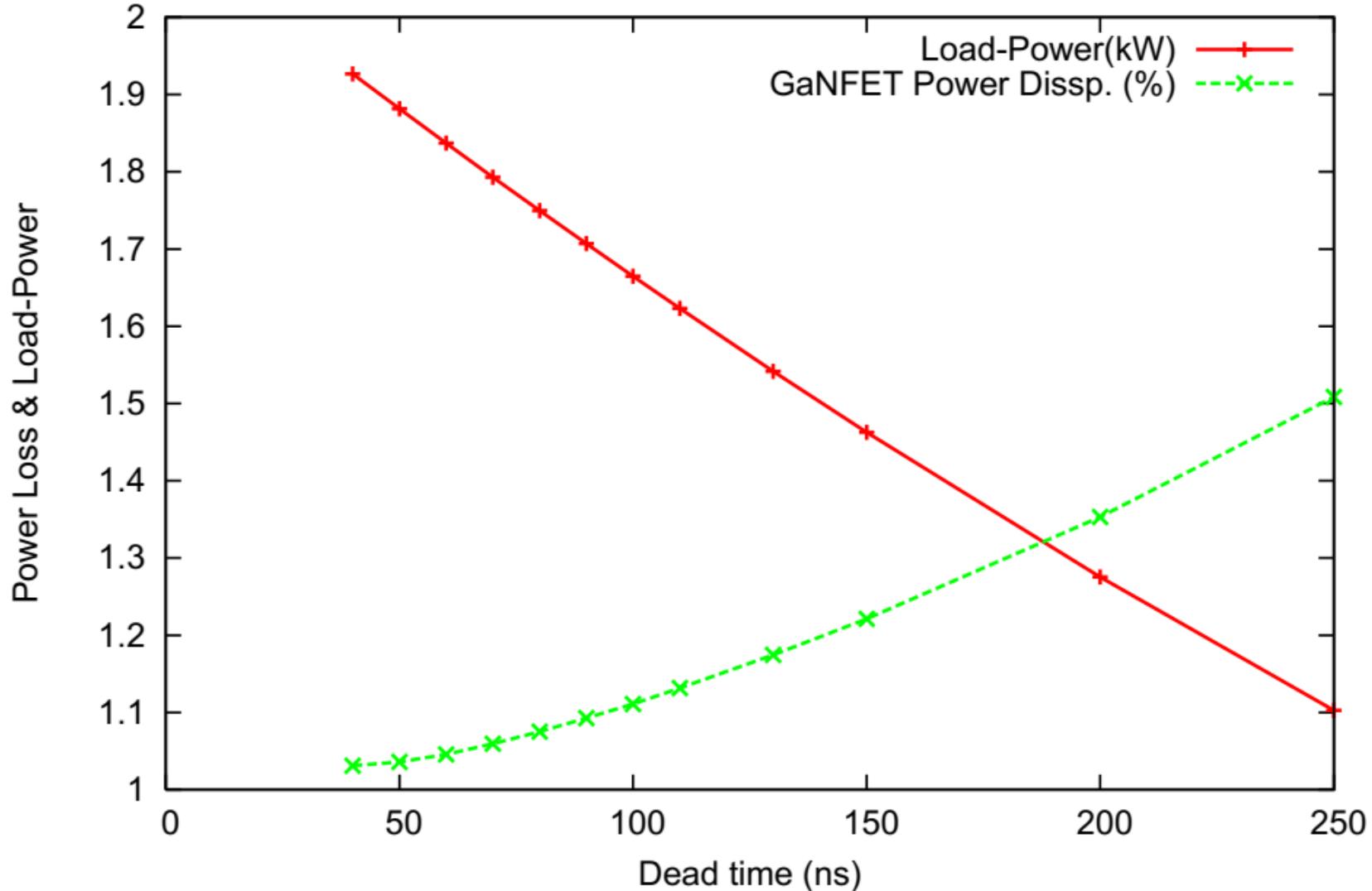1200V GaNFET Full-bridge Inverter Performance



Explanation:
 Larger dead time causes more high order oscillation or harmonic distortion of output waveforms. Power is reduced after filtering of load inductance. GaNFET power loss is also higher due to such distortion/oscillation.

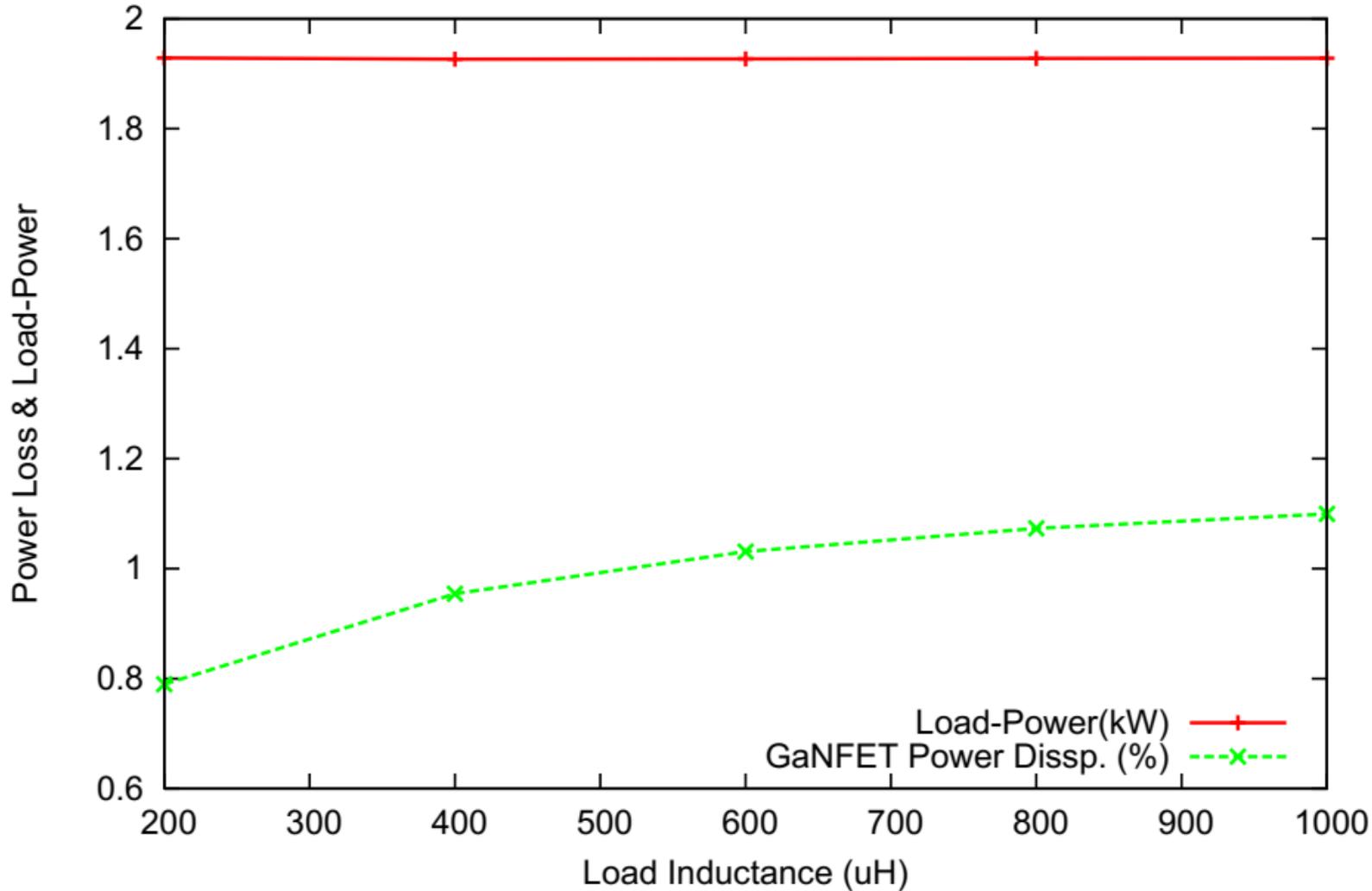1200V GaNFET Full-bridge Inverter Performance (Dead-time=40ns)



Explanation:
 Small Coss of GaNFET matches to lower load inductance in output power loop.

**Thanks for
Your Attention!**