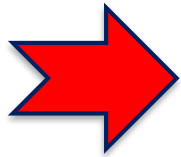


GaNPower GPI8HINOIC Application Note: LLC-DCDC & CCM Buck Converter




GANPOWER INTERNATIONAL
鎳能國際半導體有限公司

GaNPower GPI8HINOIC Application Note





**LLC DC-DC Converter (400-40V)
(1MHz)**

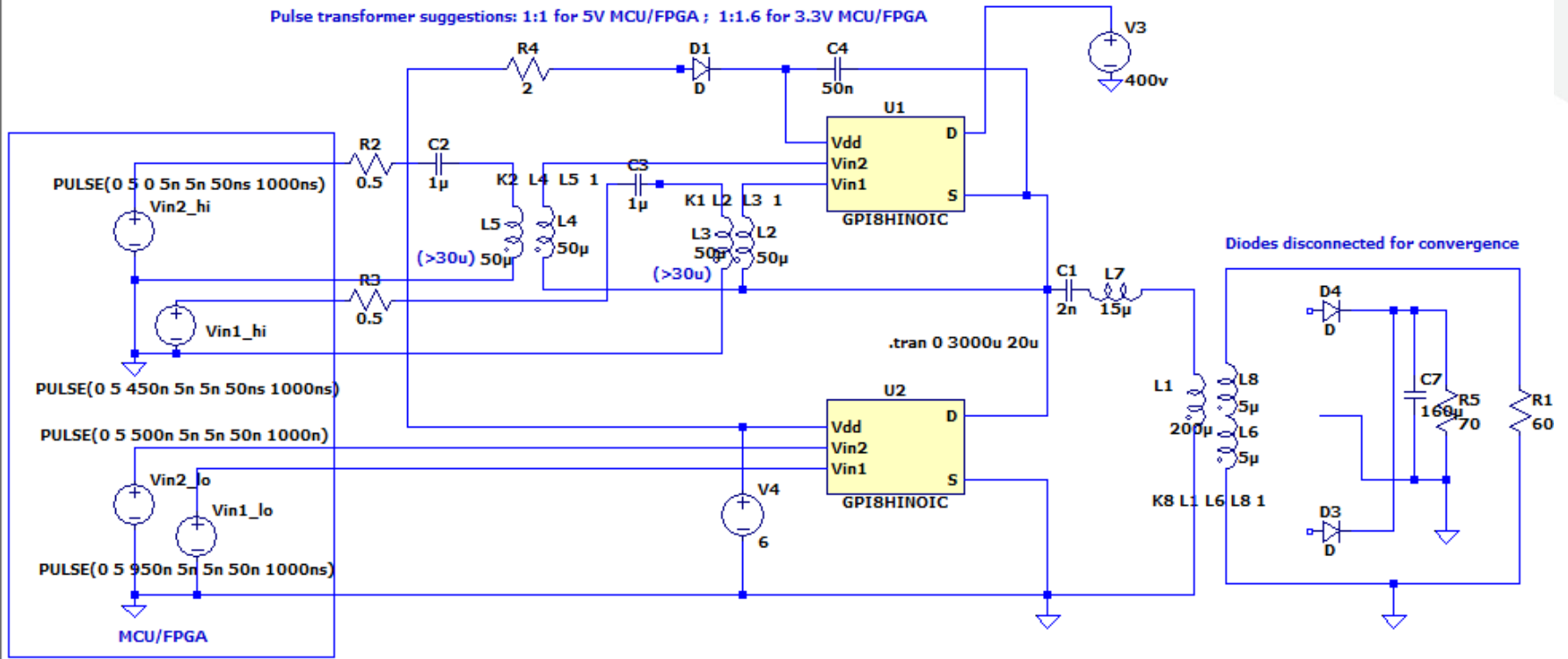
**CCM Buck Converter (400-40V)
(500KHz)**



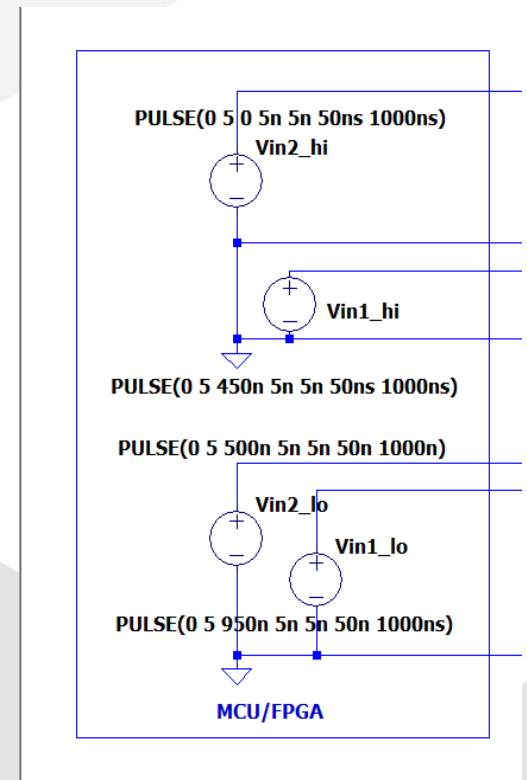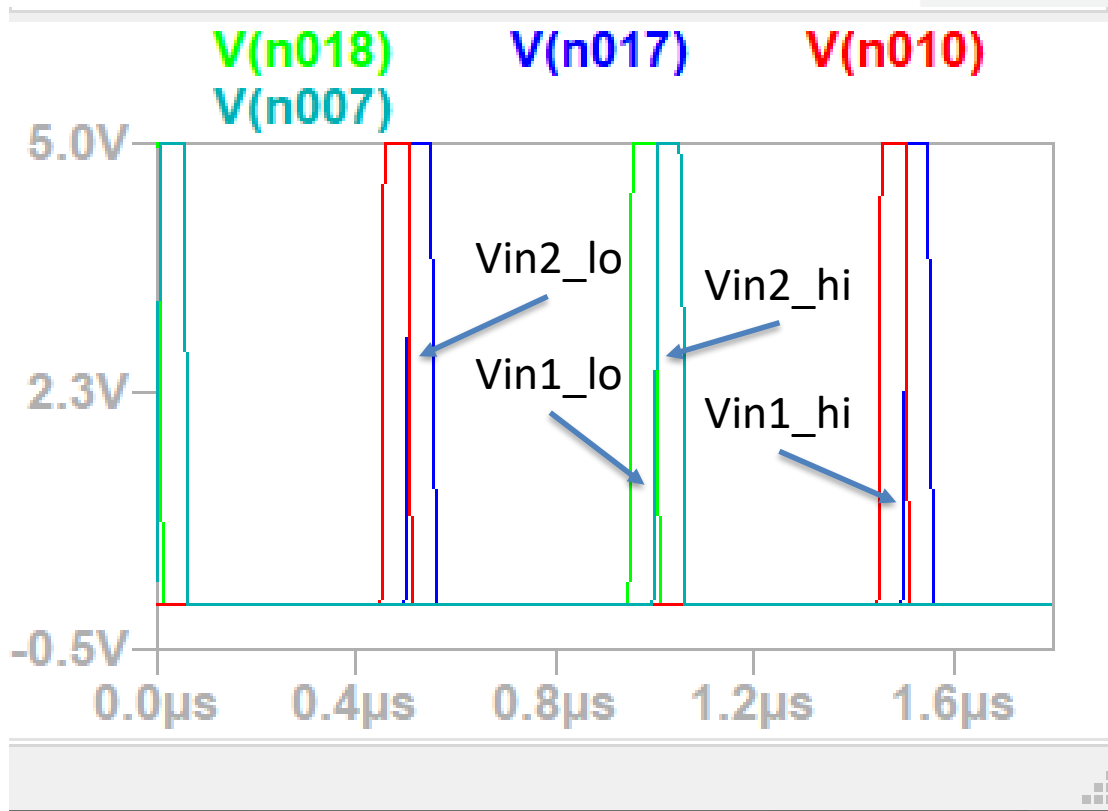
Input pulse width is fixed at 50ns regardless switching frequency. No need to adjust input coupling/level-shifting transformer when changing switching frequency.



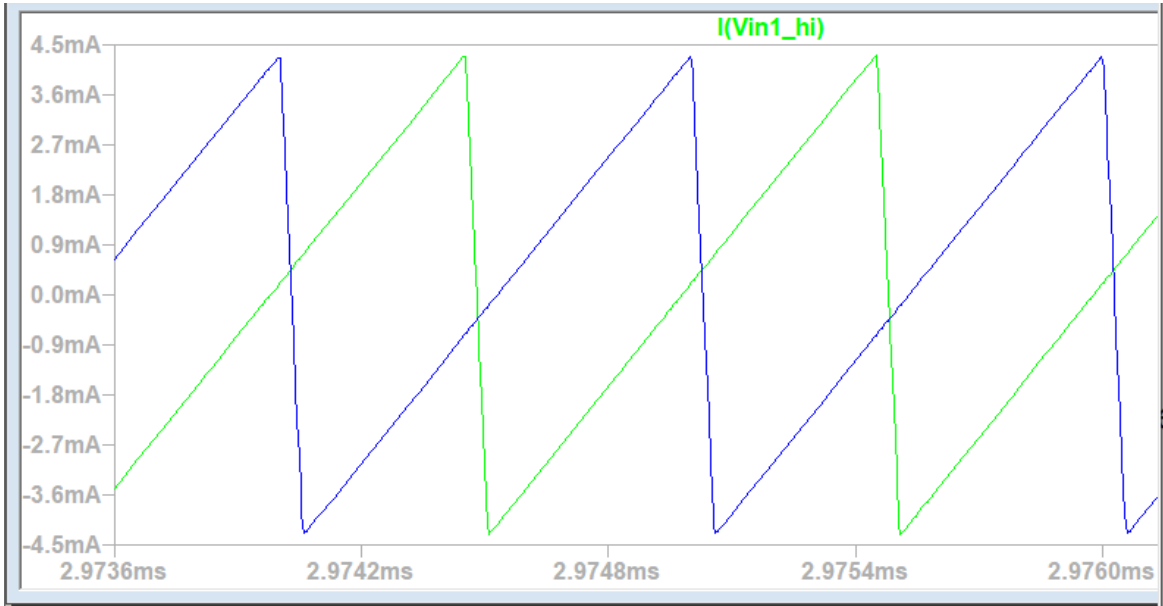Primary transformer current needed from MCU/FPGA




30uH:30uH

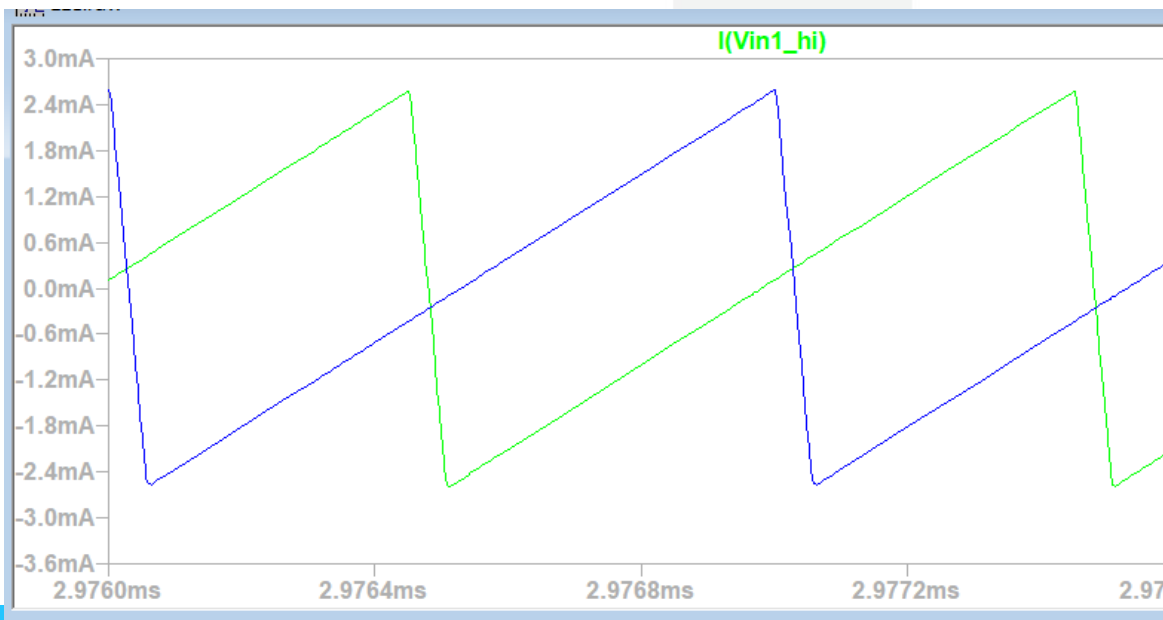


50uH:50uH

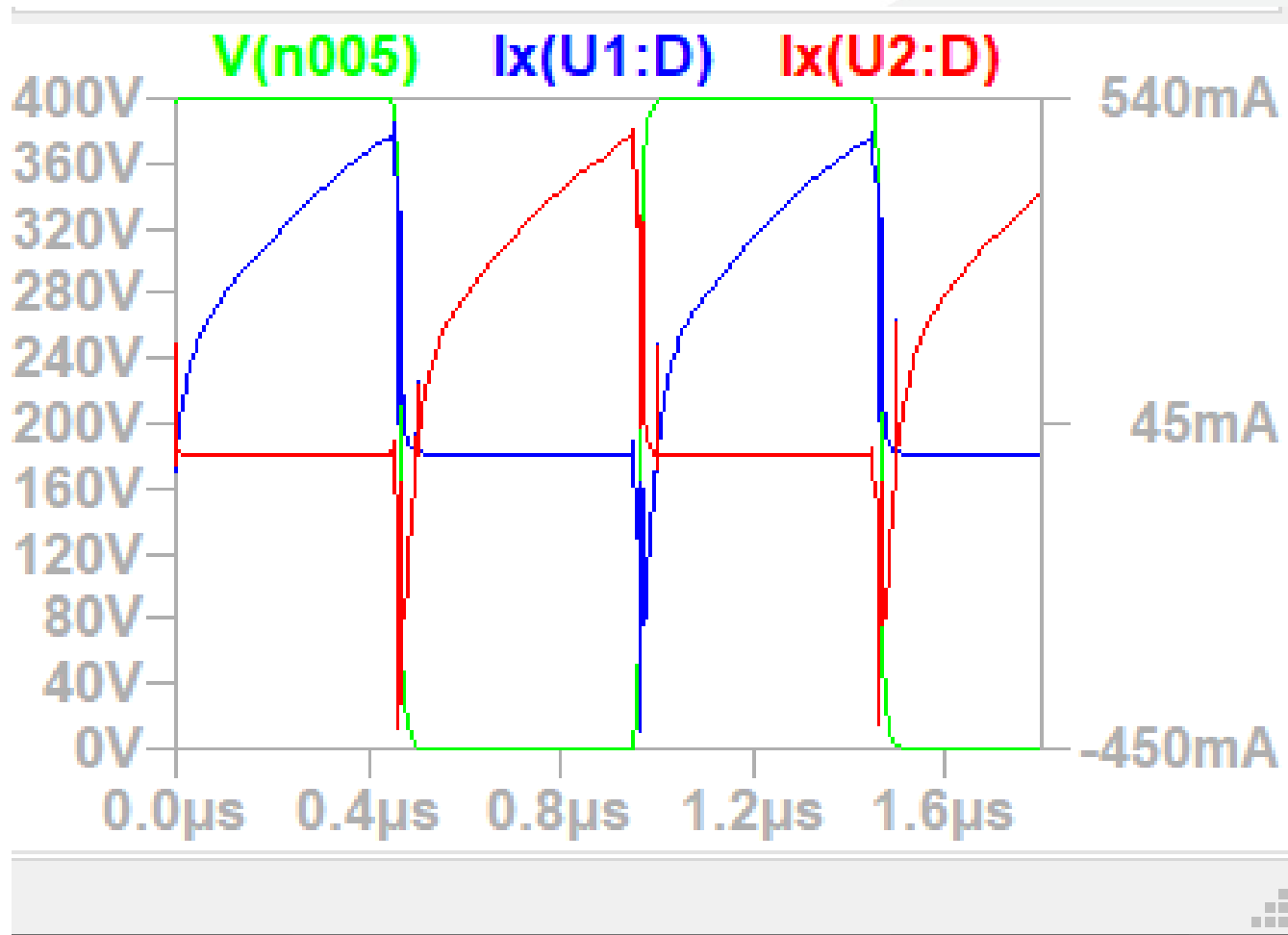Switching point voltage and IC drain currents



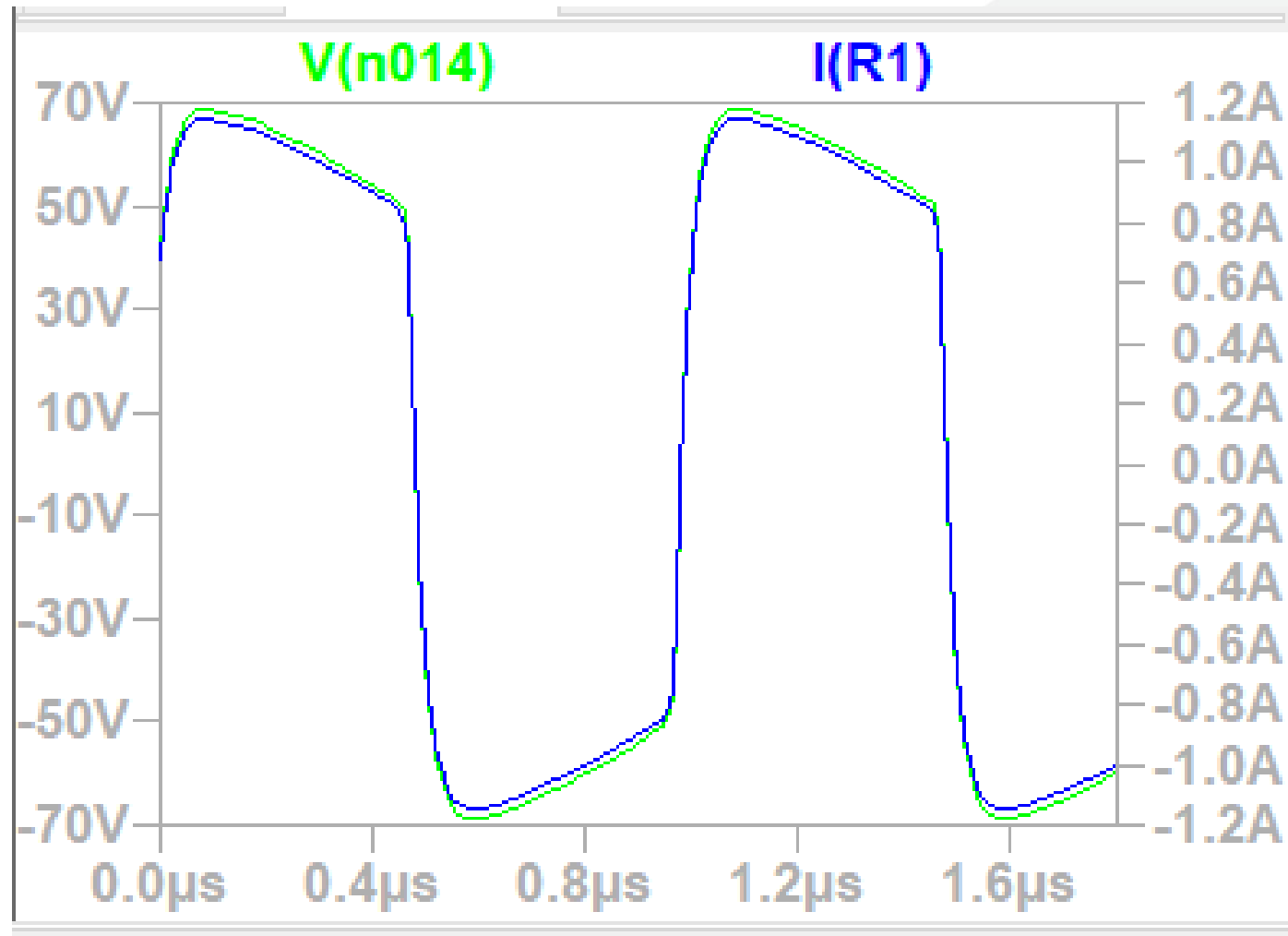Output/load voltage and current without rectifier.
Unfortunately, LTSpice does not converge with rectifier.
Hope future versions of LTSpice will converge with rectifier



GaNPower provides a half-bridge switching loss calculator program:

halfbridge_power_ltspice.exe

Welcome to GaNPower Half Bridge

Power Loss Calculator

Input control is input.txt

Please hit return to run the calculator or
enter i for information on the calculator

-->> Average $V_d \cdot I_d$ power loss:

Power loss for low side (W)= 1.463042072649182E-005

Power loss for hi side (W)= 8.509489170752462E-004

Average load power (W)= 58.8793278629851

Percent power loss= 1.470090385229909E-003

-->>

Please enter again to close the program


Summary

- GaNPower IC can be programmed using small transformer for coupling and level shifting for the high side and low side.
- Since the same narrow pulses are used for all switching frequencies, there is no need to change the transformer when changing the switching frequency.
- GaNPower IC has very low switching loss for resonant topology using half-bridge.

Thanks for your
attention!

GaNPower GPI8HINOIC Application Note


LLC DC-DC Converter (400-40V)(1MHz)

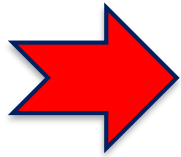



CCM Buck Converter (400-40V)(500KHz)



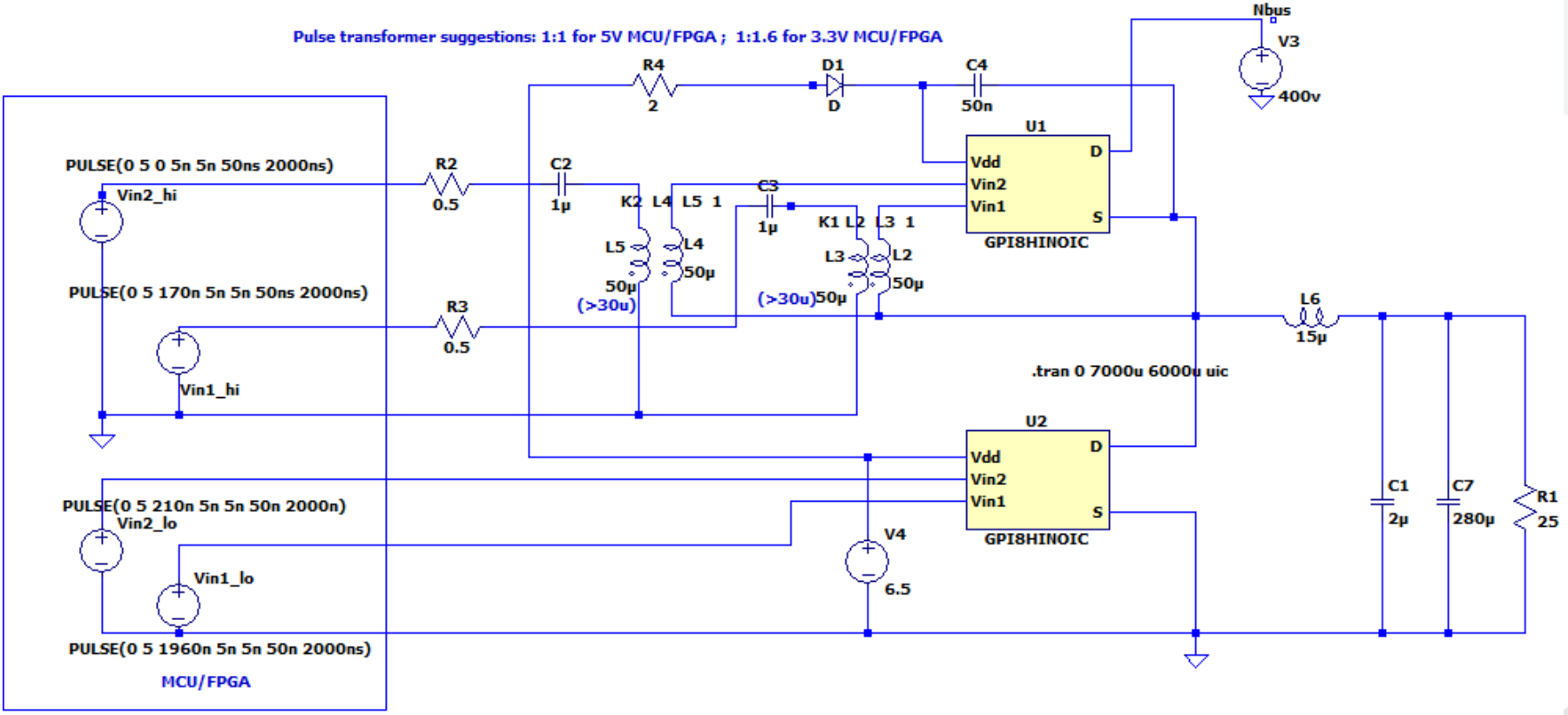
Pulse transformer suggestions: 1:1 for 5V MCU/FPGA ; 1:1.6 for 3.3V MCU/FPGA



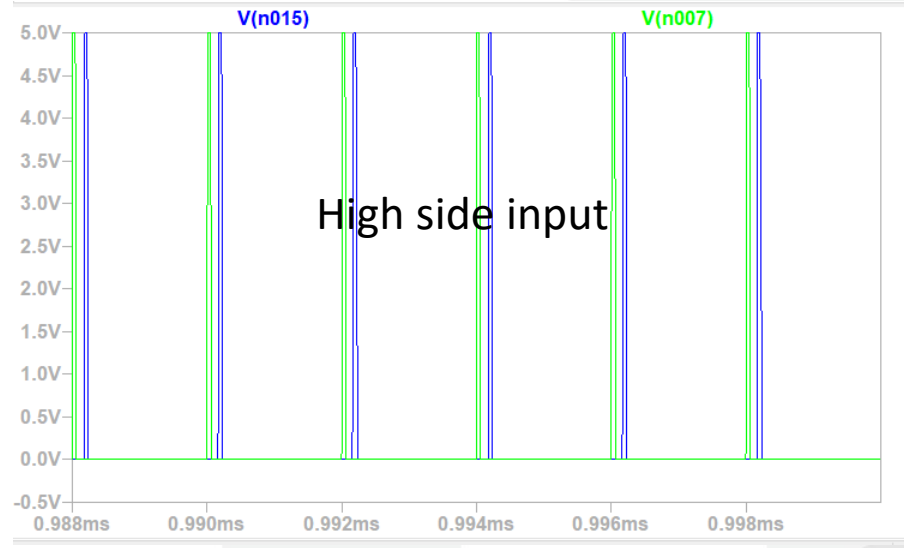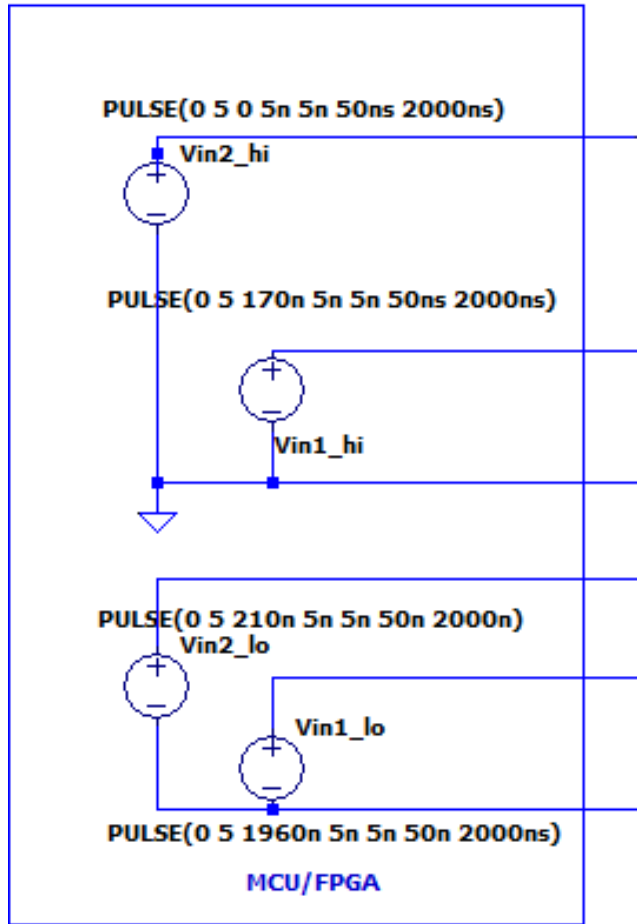
Input pulse width is fixed at 50ns regardless switching frequency. No need to adjust input coupling/level-shifting transformer when changing switching frequency.



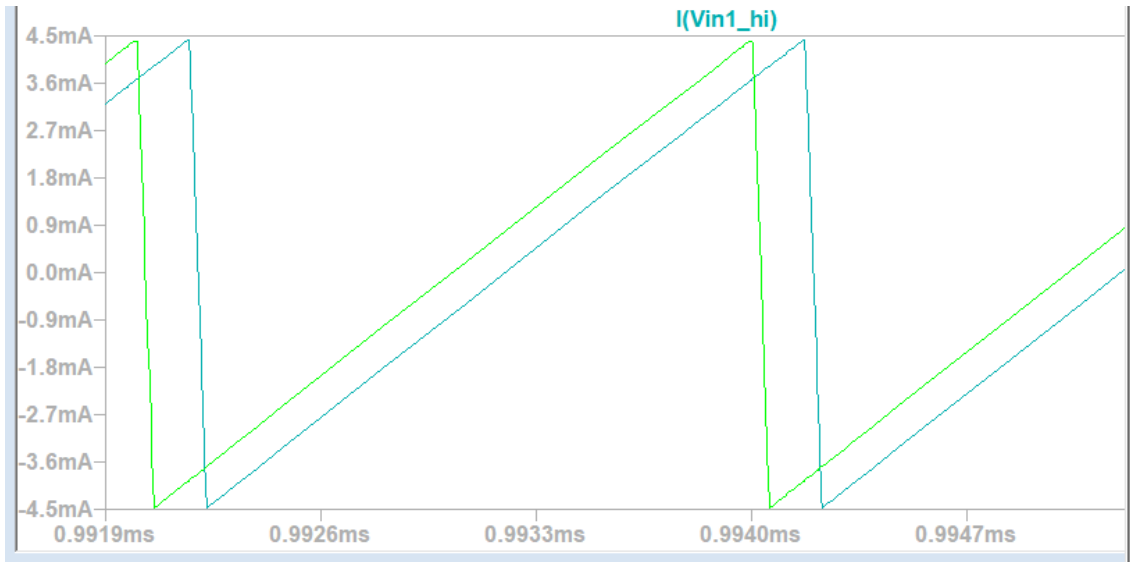Primary transformer current needed from MCU/FPGA




30uH:30uH

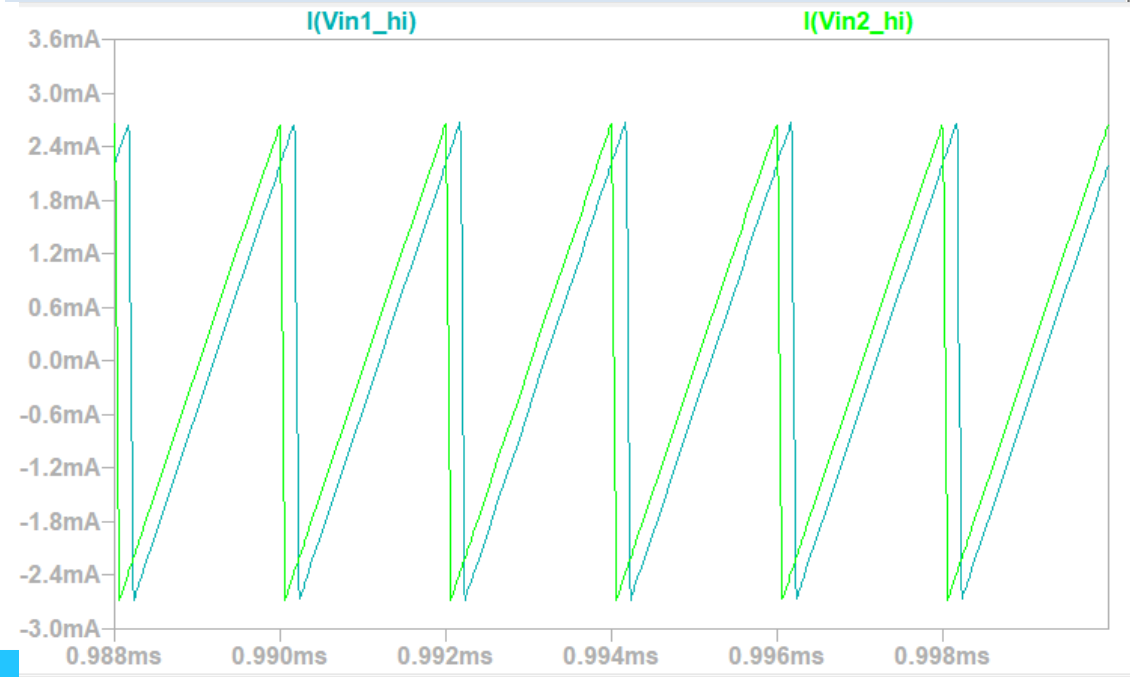


50uH:50uH

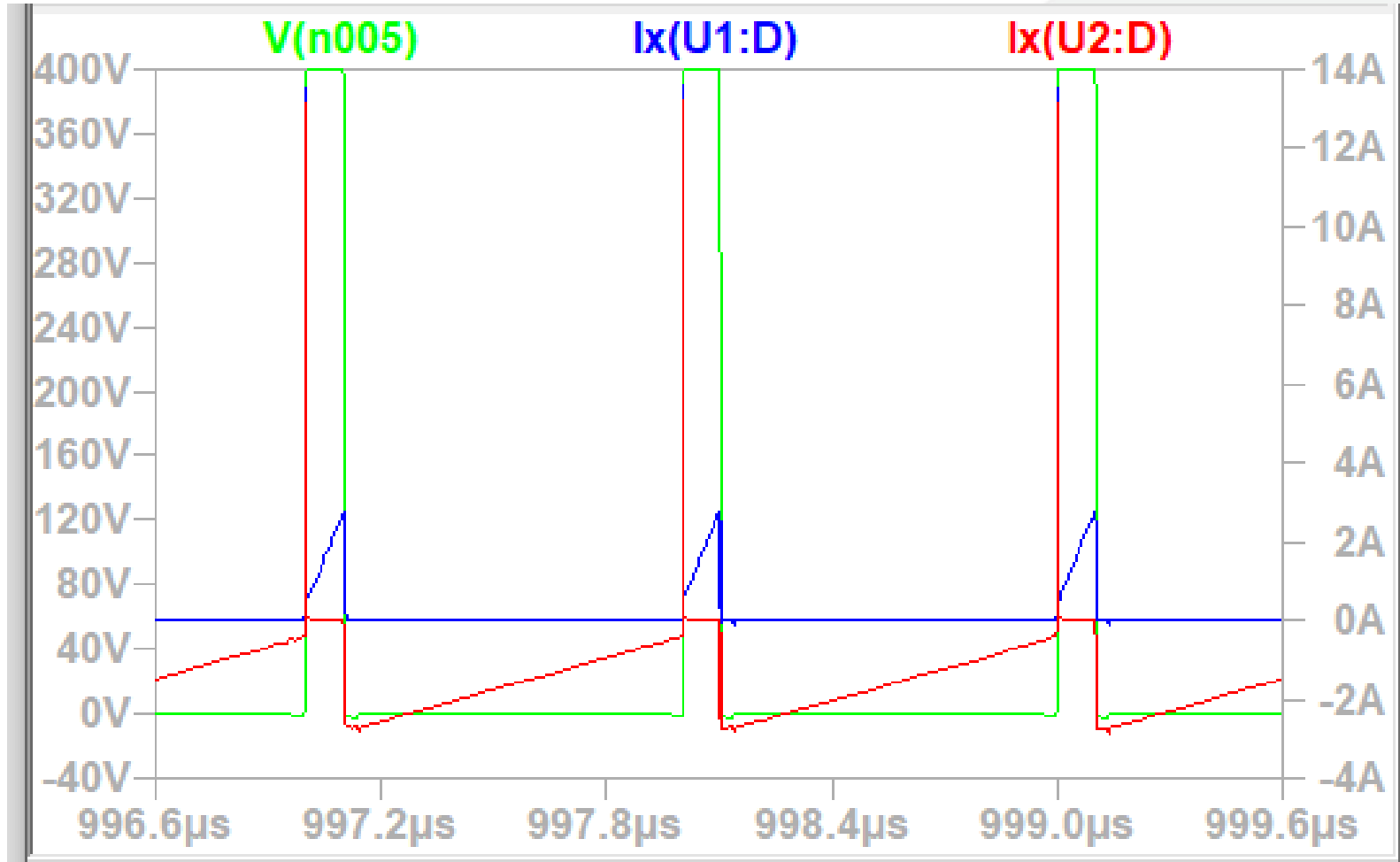Switching point voltage and IC drain currents



Output/load voltage and current

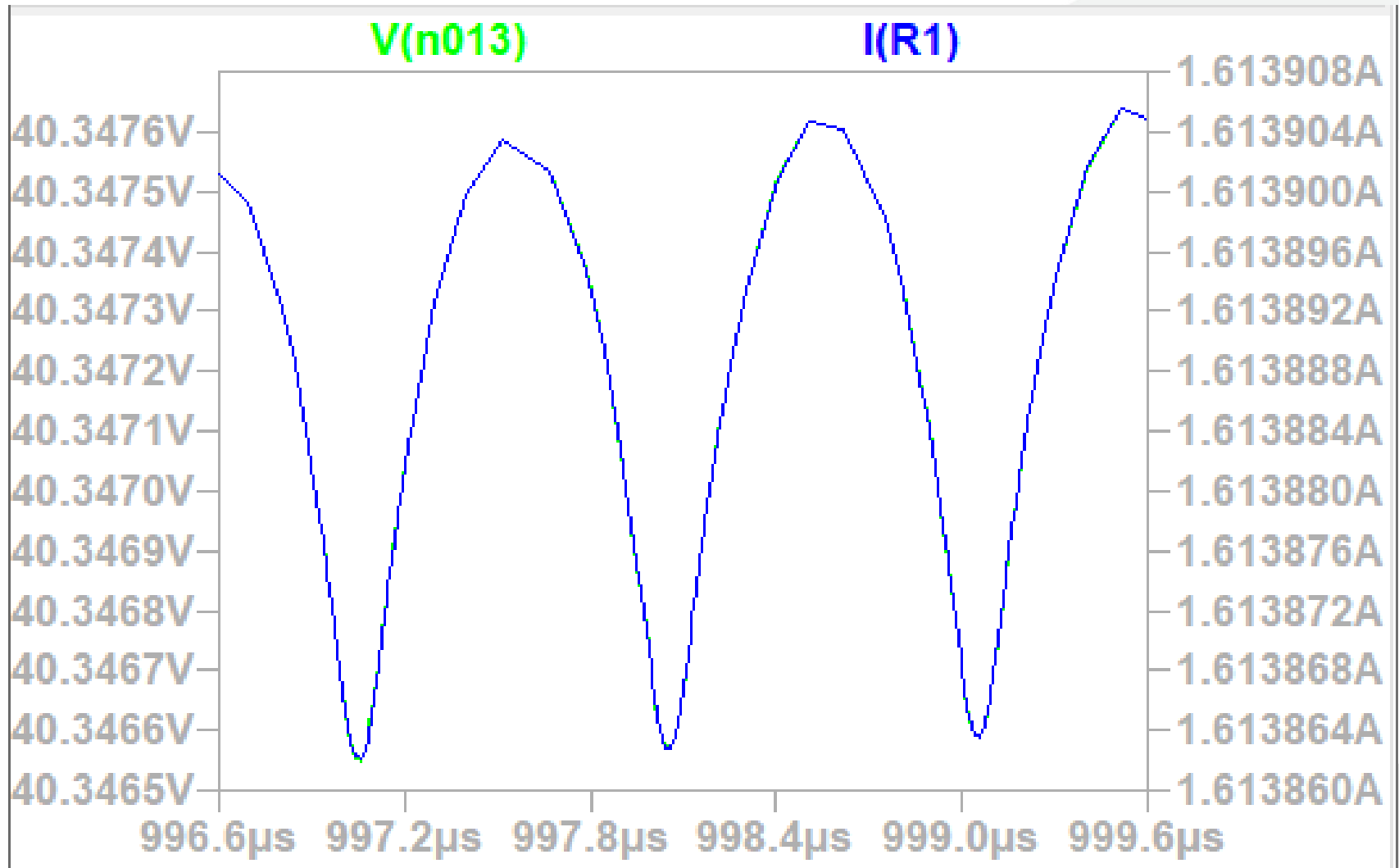

GaNPower provides a half-bridge switching loss calculator program:

halfbridge_power_ltspice.exe

Welcome to GaNPower Half Bridge

Power Loss Calculator

Input control is input.txt

Please hit return to run the calculator or
enter i for information on the calculator

-->> Average $V_d \cdot I_d$ power loss:

Power loss for low side (W)= 0.917120156146314

Power loss for hi side (W)= 7.299486461626646E-002

Average load power (W)= 64.7583131274734

Percent power loss= 1.52893886969167

-->>

Please enter again to close the program

Summary

- GaNPower IC can be programmed using small transformer for coupling and level shifting for the high side and low side.
- Since the same narrow pulses are used for all switching frequencies, there is no need to change the transformer when changing the switching frequency.
- GaN in general has higher switching loss for non-resonant / hard switching as compared with resonant topology. Special technics such as deadtime sensing/control maybe needed for high frequency switching, or lower switching frequency is advivable.

Thanks for your
attention!